

## AN1082

# Simple Design for a 4 – 20 mA Transmitter Interface Using a Motorola Pressure Sensor

Prepared by Jean Claude Hamelain  
Motorola Toulouse Application Lab Manager

### INTRODUCTION

Pressure is a very important parameter in most industrial applications such as air conditioning, liquid level sensing and flow control.

In most cases, the sensor is located close to the measured source in a very noisy environment, far away from the receiver (recorder, computer, automatic controller, etc.)

The transmission line can be as long as a few hundred meters and is subject to electromagnetic noise when the signal is transmitted as voltage. If the signal is transmitted as a current it is easier to recover at the receiving end and is less affected by the length of the transmission line.

The purpose of this note is to describe a simple circuit which can achieve high performances, using standard Motorola pressure sensors, operational amplifiers and discrete devices.

### PERFORMANCES

The following performances have been achieved using an MPX2100DP Motorola pressure sensor and an MC33079 quad operational amplifier. The MPX2100DP is a 100 kPa temperature compensated differential pressure sensor. The load is a 150 ohm resistor at the end of a 50 meter telephone line. The 15 volt power supply is connected at the receiver end.

Power Supply	+15 Vdc 30 mA
Connecting Line	3 wire telephone cable
Load Resistance	150 to 400 Ohms
Temperature Range	–40 to +85°C (up to +125°C with special hardware)
Pressure Range	0 to 200 kPa (2 bars — with appropriate pressure sensor)
Total Maximum Error	Better than 2% full scale

### Basic Circuit

The Motorola MPX2100DP pressure sensor is a very high performance piezo resistive pressure sensor. Manufacturing technologies include standard bipolar processing techniques with state of the art metalization and on-chip laser trim for off-set and temperature compensation.

This unique design, coupled with computer LASER trimming, gives this device excellent performance at competi-

tive cost for demanding applications such as automotive, industrial or medical.

MC33078, 79 operational amplifiers are specially designed for very low input voltage, a high output voltage swing and very good stability versus temperature changes.

### First Stage

The Motorola MPX2100 and the operational amplifier are directly powered by the 15 Vdc source. The first stage is a simple true differential amplifier made with both of the operational amplifiers in the MC33078. The potentiometer,  $R_G$ , provides adjustment for the output.

This first stage is available as a pressure sensor kit, SEK-1 (refer to EB130/D). If using the kit, the resistors must be changed according to the schematic bellow to provide a full 4 – 20 mA output.

### Current Generator

The voltage to current conversion is made with a unity gain differential amplifier, one of the four operational amplifiers in an MC33079. The two output connections from the first stage are connected to the input of this amplifier through  $R_3$  and  $R_5$ . Good linearity is achieved by the matching between  $R_3$ ,  $R_4$ ,  $R_5$  and  $R_6$ , providing a good common mode rejection. For the same reason, a good match between resistors  $R_8$  and  $R_9$  is needed.

The MC33078 or MC33079 has a limited current output, therefore a 2N2222 general purpose transistor is connected as the actual output current source to provide a 20 mA output.

To achieve good performance with a very long transmission line it may be necessary to place some capacitors ( $C_1$ ,  $C_2$ ) between the power supply and output to prevent oscillations.

### Calibration


The circuit is electrically connected to the 15 Vdc power supply and to the load resistor (receiver).

The high pressure is connected to the pressure port and the low pressure (if using a differential pressure sensor), is connected to the vacuum port.

It is important to perform the calibration with the actual transmission line connected.



**MOTOROLA**

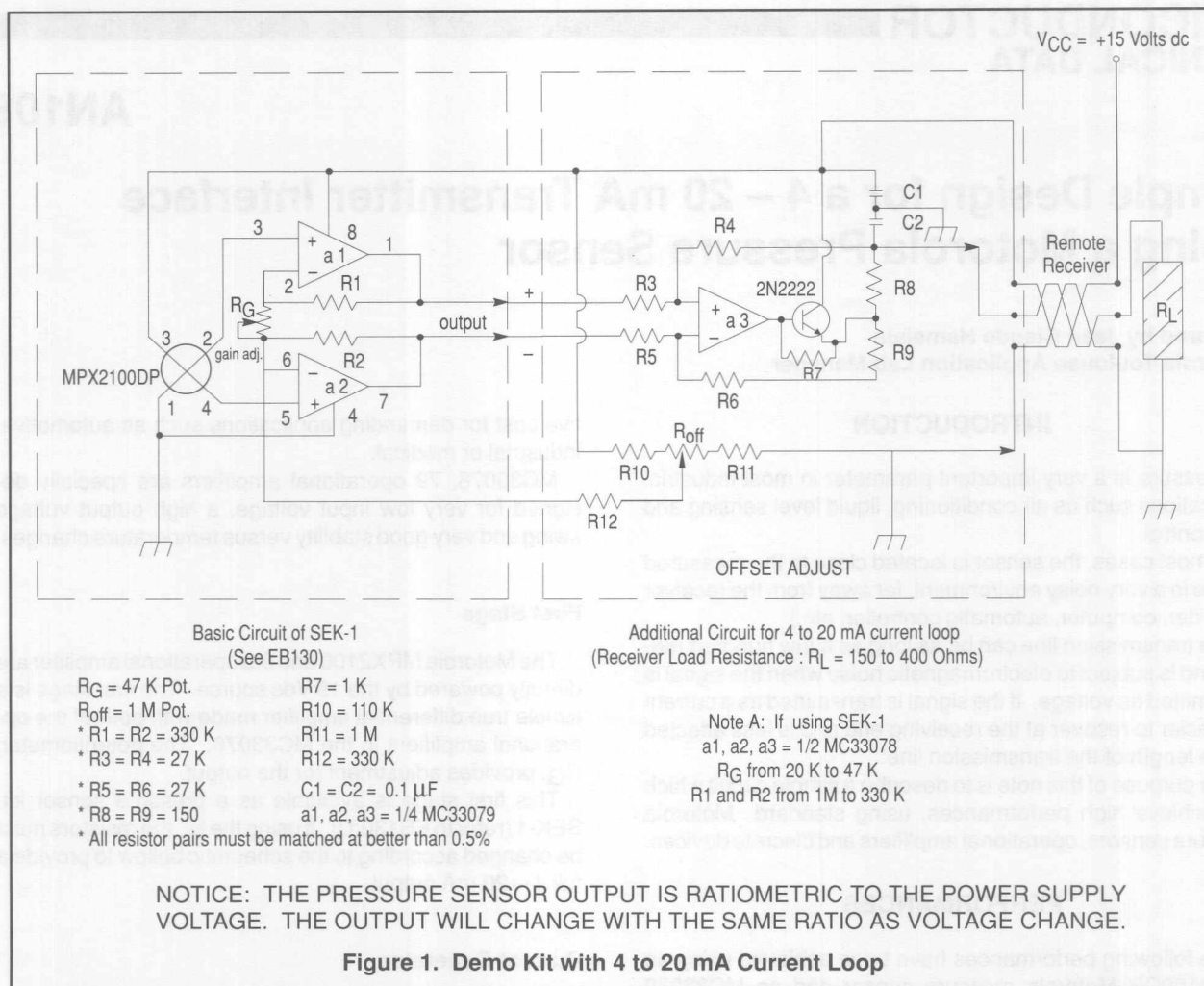

To achieve good performance with a very long transmission line it may be necessary to place some capacitors ( $C_1, C_2$ ) between the power supply and output to prevent oscillations.

#### Calibration

The circuit is electrically connected to the 15 Vdc power supply and to the load resistor (receiver).

The high pressure is connected to the pressure port and the low pressure (if using a differential pressure sensor), is connected to the vacuum port.

It is important to perform the calibration with the actual transmission line connected.

The circuit needs only two adjustments to achieve the 4 – 20 mA output current.

1. With no pressure (zero differential pressure), adjust  $R_{off}$  to read exactly 4 mA on the receiver.

2. Under the full scale pressure, adjust  $R_G$  to exactly read 20 mA on the receiver. The calibration is now complete.

The output is ratiometric to the power supply voltage. For example, if the receiver reads 18 mA at 80 kPa and 15 V power supply, the receiver should read 16.8 mA under the same

pressure with 14 V power supply.

For best results it is mandatory to use a regulated power supply. If that is not possible, the circuit must be modified by inserting a 12 V regulator to provide a constant supply to the pressure sensor.

When using a Motorola MC78L12AC voltage regulator the circuit can be used with power voltage variation from 14 to 30 volts.

The following results have been achieved using an MPX2100DP and two MC33078s. The resistors were regular carbon resistors, but pairs were matched at  $\pm 0.3\%$  and capacitors were  $0.1$   $\mu$ F. The load was 150 ohms and the transmission line was a two pair telephone line with the +15 Vdc power supply connected on the remote receiver side.

Note: Best performances in temperature can be achieved using metal film resistors. The two potentiometers must be chosen for high temperatures up to  $125^\circ\text{C}$ .

The complete circuit with pressure sensor is available under reference TZA120 and can be ordered as a regular Motorola product for evaluation.

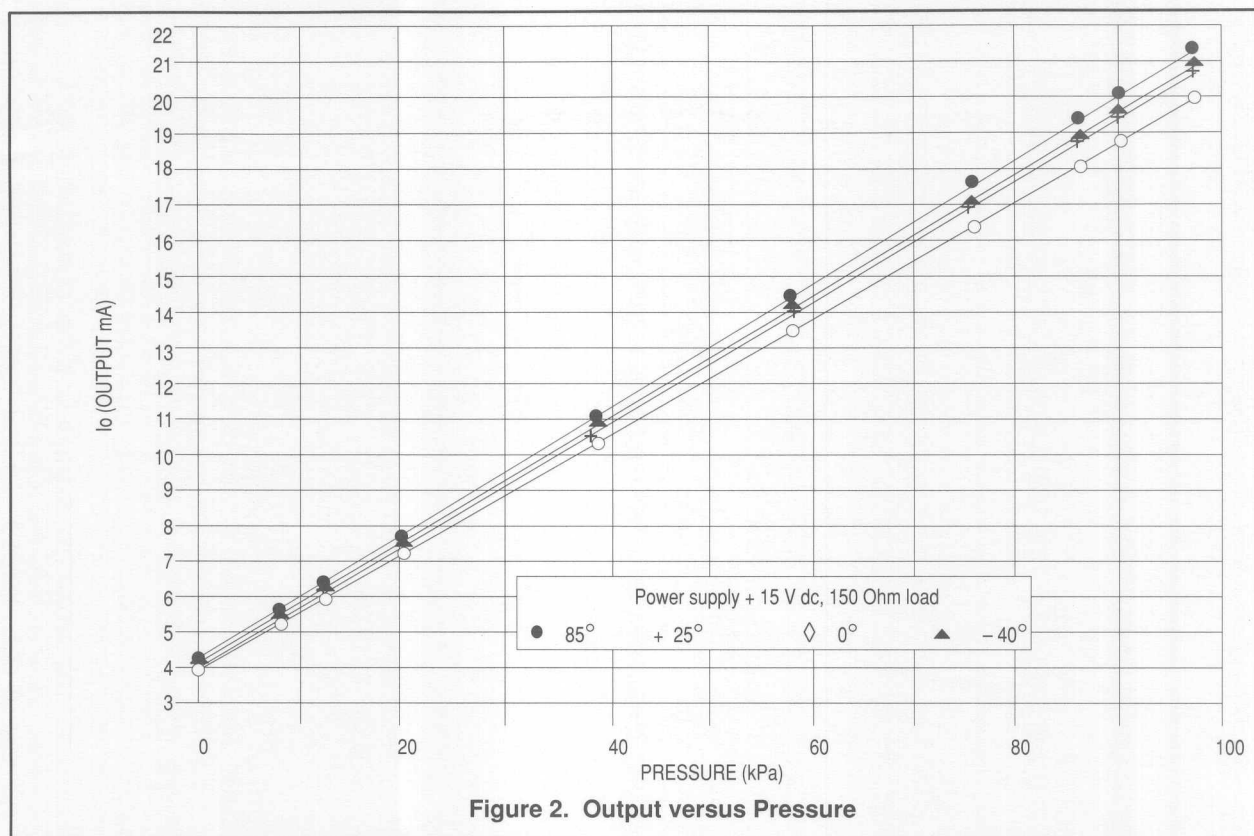


Figure 2. Output versus Pressure

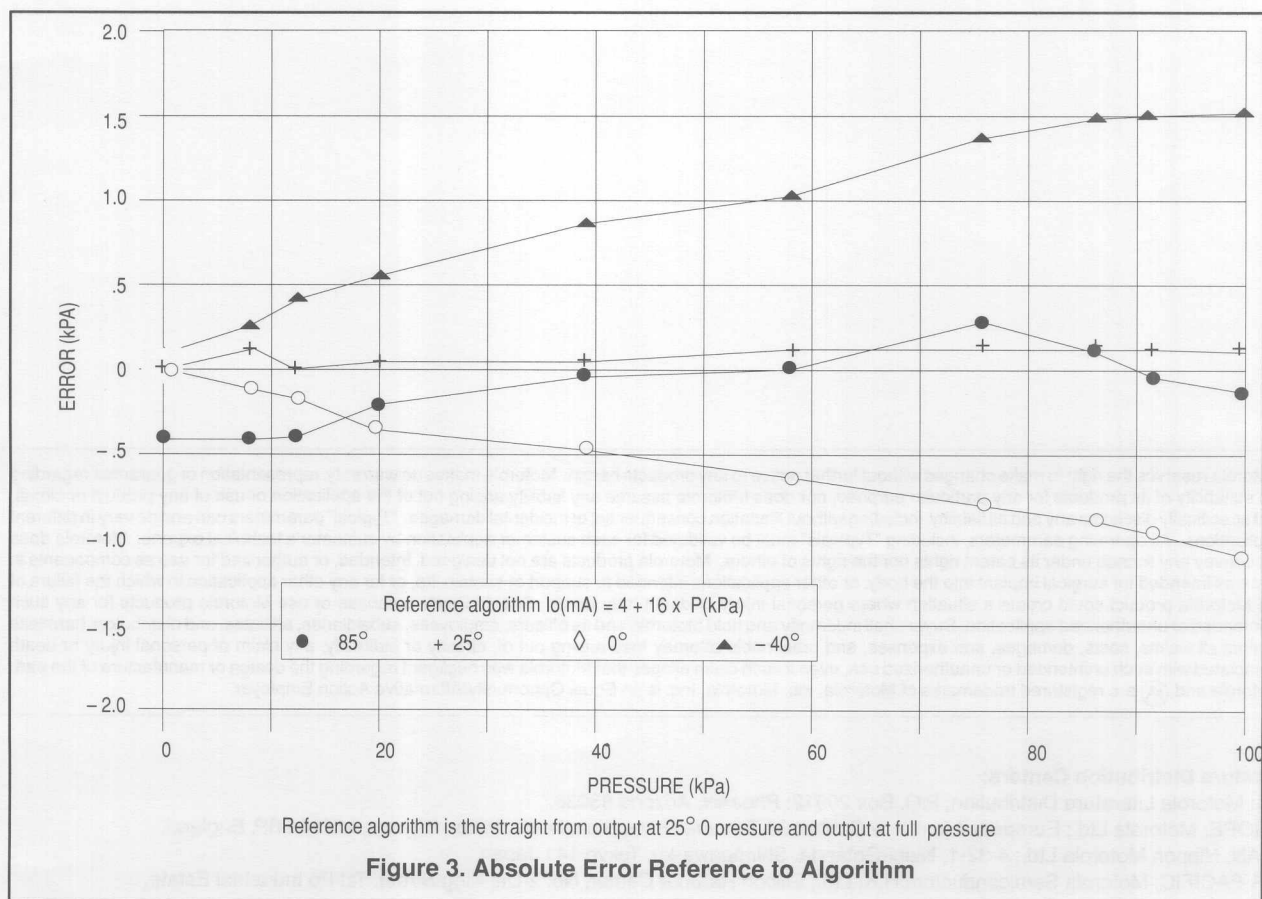


Figure 3. Absolute Error Reference to Algorithm